

Template Week 2 - Logic

Student number: 582840

Assignment 2.1: Parking lot

Which gates do you need?

Een AND gate

Complete this table

Parking lot 1	Parking lot 2	Parking lot 3	Result (full)
0	0	0	0
0	0	1	0
0	1	0	0
1	0	0	0
0	1	1	0
1	1	0	0
1	0	1	0
1	1	1	1

Assignment 2.2: Android or iPhone

Which gates do you need?

Een NOR gate

Complete this table

Android phone	iPhone	Result (Phone in possession)
0	0	Geen
1	0	Android
0	1	iPhone
1	1	Geen

Assignment 2.3: Four NAND gates

Complete this table

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0


How can the design be simplified?

Door een NOR gate

Assignment 2.4: Getting to know Logisim evolution

Screenshot of the design with your name and student number in it:


Bas van Eijk 582840

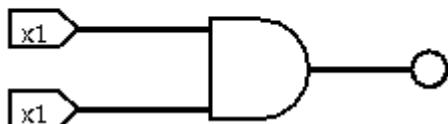

Assignment 2.5: SR Latch

Screenshot SR Latch in Logisim with your name and student number:


Bas van Eijk 582840

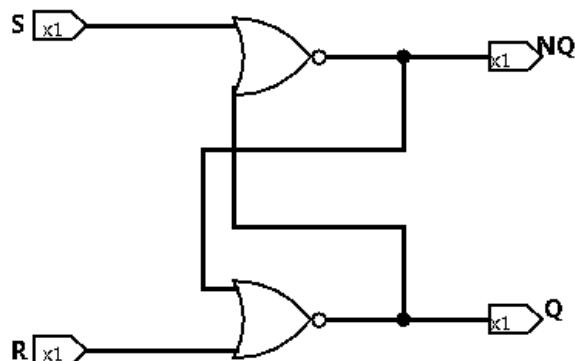

Assignment 2.6: Vending Machine

Screenshot Vending Machine in Logisim with your name and student number:

Bas van Eijk 582840

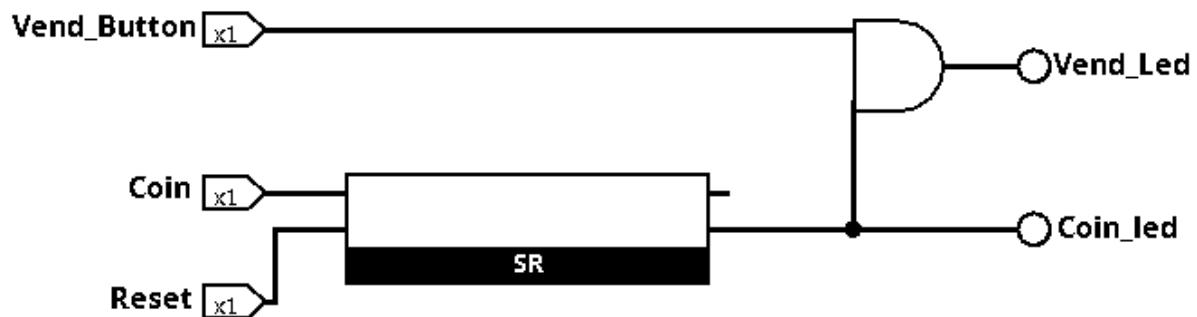

Assignment 2.7: Bitwise operators

Complete the java source code for bitwise operators. Put the source code here.

```
#1  
public class Main {  
    public static void main(String[] args) {  
        int number = 5;  
        if ((number & 1) == 1) System.out.println("Number is odd");  
        else System.out.println("number is even");  
    }  
}
```

#2

```
public class Main {  
    public static void main(String[] args) {  
        int number = 1;  
        if ((number & (number - 1)) == 0) System.out.println("Number is a power of 2");  
        else System.out.println("number isn't a power of 2");  
    }  
}
```

#3

```
public class Main {  
    public static void main(String[] args) {  
        final int READ = 4;  
        final int WRITE = 2;  
        final int EXECUTE = 1;  
        int userPermissions = 7;  
        if((userPermissions & READ) != 0) System.out.println("User has read permissions");  
        else System.out.println("User can't read. No permissions.");  
    }  
}
```

#4

```
public class Main {  
    public static void main(String[] args) {  
        final int READ = 4;  
        final int WRITE = 2;  
        final int EXECUTE = 1;  
  
        int userPermissions = 0;  
  
        // Geef de gebruiker READ en EXECUTE permissies  
        userPermissions = READ | EXECUTE;  
  
        System.out.println("User permissions: " + userPermissions);  
    }  
}
```

#5

```
public class Main {  
    public static void main(String[] args) {  
        final int READ = 4;  
        final int WRITE = 2;  
        final int EXECUTE = 1;  
  
        int userPermissions = 6;  
  
        userPermissions = userPermissions ^ WRITE;  
  
        System.out.println("User permissions: " + userPermissions);  
    }  
}
```

```
#6
public class Main {
    public static void main(String[] args) {
        int number = 5;

        number = ~number + 1;

        System.out.println("Number: " + number);
    }
}
```

Assignment 2.8: Java Application Bit Calculations

Create a java program that accepts user input and presents a menu with options.

1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number?

Implement the methods by using the bitwise operators you have just learned.

Organize your source code in a readable manner with the use of control flow and methods.

Keep this application because you need to expand it in week 6 for calculating network segments.

Paste source code here, with a screenshot of a working application.

```
import java.util.Scanner;

public class Main {

    public static void main(String[] args) {
        Scanner scanner = new Scanner(System.in);

        System.out.print("Enter a number: ");
        int number = scanner.nextInt();

        System.out.println("\nChoose an option:");
        System.out.println("1. Is number odd?");
        System.out.println("2. Is number a power of 2?");
        System.out.println("3. Two's complement of number");
        System.out.print("Option: ");
        int option = scanner.nextInt();
```

```

switch(option) {
    case 1:
        if (isOdd(number)) {
            System.out.println(number + " is odd.");
        } else {
            System.out.println(number + " is even.");
        }
        break;
    case 2:
        if (isPowerOfTwo(number)) {
            System.out.println(number + " is a power of 2.");
        } else {
            System.out.println(number + " is not a power of 2.");
        }
        break;
    case 3:
        int twosComp = twosComplement(number);
        System.out.println("Two's complement: " + twosComp);
        break;
    default:
        System.out.println("Invalid option.");
}

scanner.close();
}

public static boolean isOdd(int n) {
    return (n & 1) != 0;
}

public static boolean isPowerOfTwo(int n) {
    return n > 0 && (n & (n - 1)) == 0;
}

public static int twosComplement(int n) {
    return ~n + 1;
}

```

```
/home/bas/.jdks/ms-21.0.8/bin/java -javaagent:/home/bas/.local/share/JetBrains/Toolbox/apps/intelliij-idea-ultimate/lib/idea_rt.jar=32805 -Dfile.encoding=UTF-8
Enter a number: 3

Choose an option:
1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number
Option: 1
3 is odd.

Process finished with exit code 0
```

> src >  Main >  isOdd

```
/home/bas/.jdks/ms-21.0.8/bin/java -javaagent:/home/bas/.local/share/JetBrains/Toolbox/apps/intelliij-idea-ultimate/lib/idea_rt.jar=33127 -Dfile.encoding=UTF-8
Enter a number: 8

Choose an option:
1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number
Option: 2
8 is a power of 2.

Process finished with exit code 0
```

> src >  Main >  isOdd

```
/home/bas/.jdks/ms-21.0.8/bin/java -javaagent:/home/bas/.local/share/JetBrains/Toolbox/apps/intelliij-idea-ultimate/lib/idea_rt.jar=34129 -Dfile.encoding=UTF-8
Enter a number: 3

Choose an option:
1. Is number odd?
2. Is number a power of 2?
3. Two's complement of number
Option: 3
Two's complement: -3

Process finished with exit code 0
```

> src >  Main >  isOdd

Ready? Then save this file and export it as a pdf file with the name: [week2.pdf](#)